



<https://i.pinimg.com/236x/9f/7c/42/9f7c42a12a59e2706b144d62d9b67f4e.jpg>

Lecture 4:


Basic Processor Architecture

Some slides adapted from Mary Jane Irwin at Penn State University for *Computer Organization and Design*, Patterson & Hennessy,
© 2005


Review: CPU Performance

- execution time = seconds / program

 
$$\frac{\text{Instructions}}{\text{program}} \times \frac{\text{cycles}}{\text{Instruction}} \times \frac{\text{seconds}}{\text{cycle}}$$



 - programmer
- algorithms
- ISA
- compilers



 - microarchitecture
- system architecture



- microarchitecture
pipeline depth
- circuit design
- technology

Review: Amdahl's Law

- law of diminishing returns


- ✓ make the common case faster

- ✓ speedup = $\text{Perf}_{\text{new}} / \text{Perf}_{\text{old}} = T_{\text{old}} / T_{\text{new}} =$

$$\frac{1}{(1-f) + \frac{f}{P}}$$

 - example

- ✓ supposing floating point instructions are improved to run 2X but comprise only 10% of actual instructions, what's the speedup?




Processor: Datapath & Control

□ our implementation of a processor is simplified

- memory-reference instructions: **lw, sw**
- arithmetic/logical instructions: **add, sub, and, or, slt**
- branch instructions: **beq, j**

□ generic implementation

 - use the program counter (PC) to supply the instruction address and fetch the instruction from memory (and update the PC)
- decode the instruction (and read registers)
- execute the instruction




 
□ all instructions (except **j**) use the ALU after reading the registers

Recap: Instruction Execution

- ❑ PC → instruction memory, fetch instruction
- ❑ register numbers → register file, read registers
- ❑ depending on instruction class
 - use ALU to calculate
 - arithmetic result
 - memory address for load/store
 - branch target address
 - access data memory for load/store
 - PC ← target address or PC + 4


Clocking Methodologies

- ❑ clocking methodology defines when signals can be read and when they are written
 - edge-triggered methodology
 - ❑ typical execution
 - read contents of state elements
 - send values through combinational logic
 - write results to one or more state elements
- 




- ❑ assumes state elements are written on every clock cycle; if not, need explicit write control signal
 - write occurs only when both the write control is asserted and the clock edge occurs

Overview (Simplified example circuit)

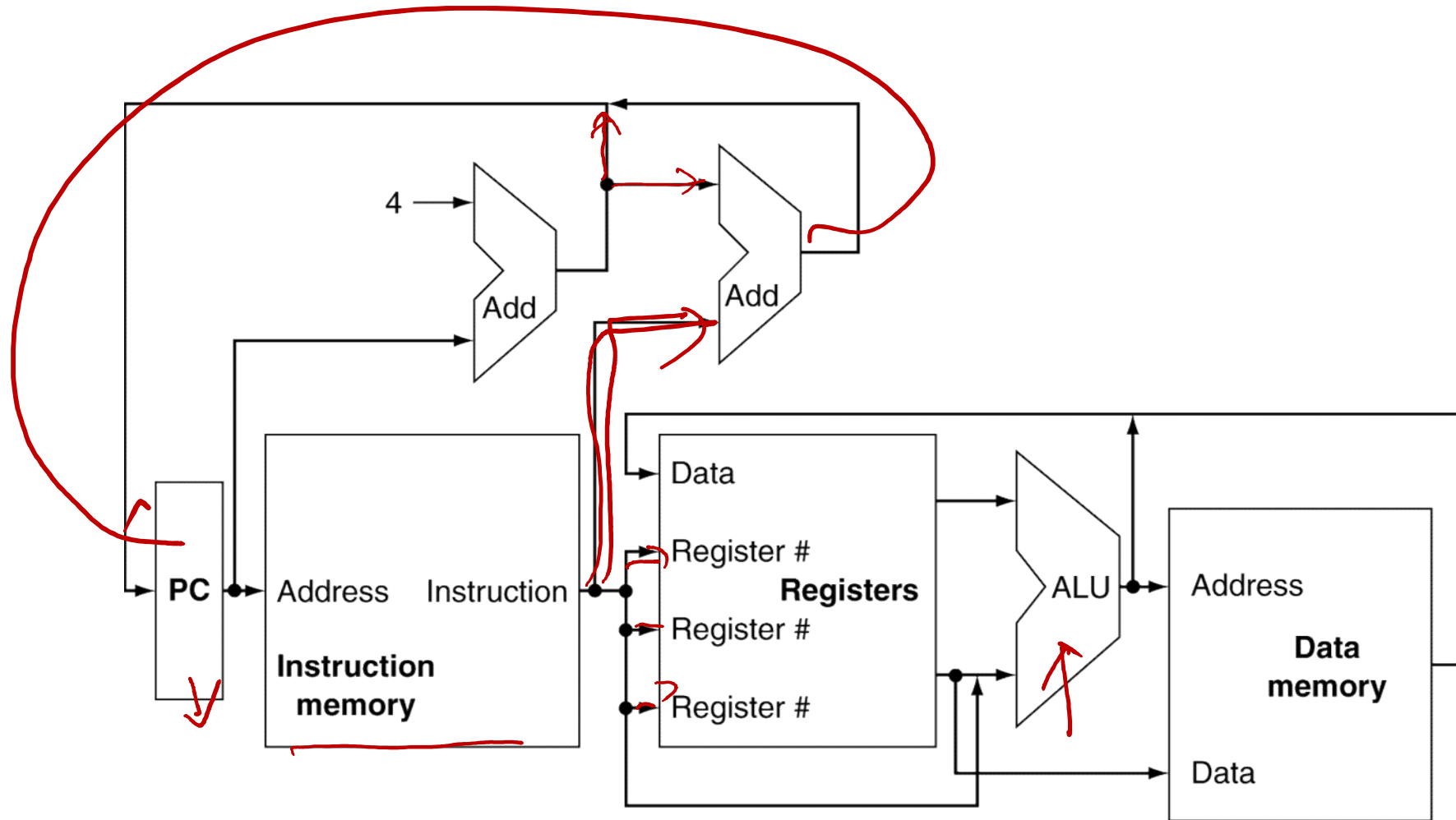

Multiplexers

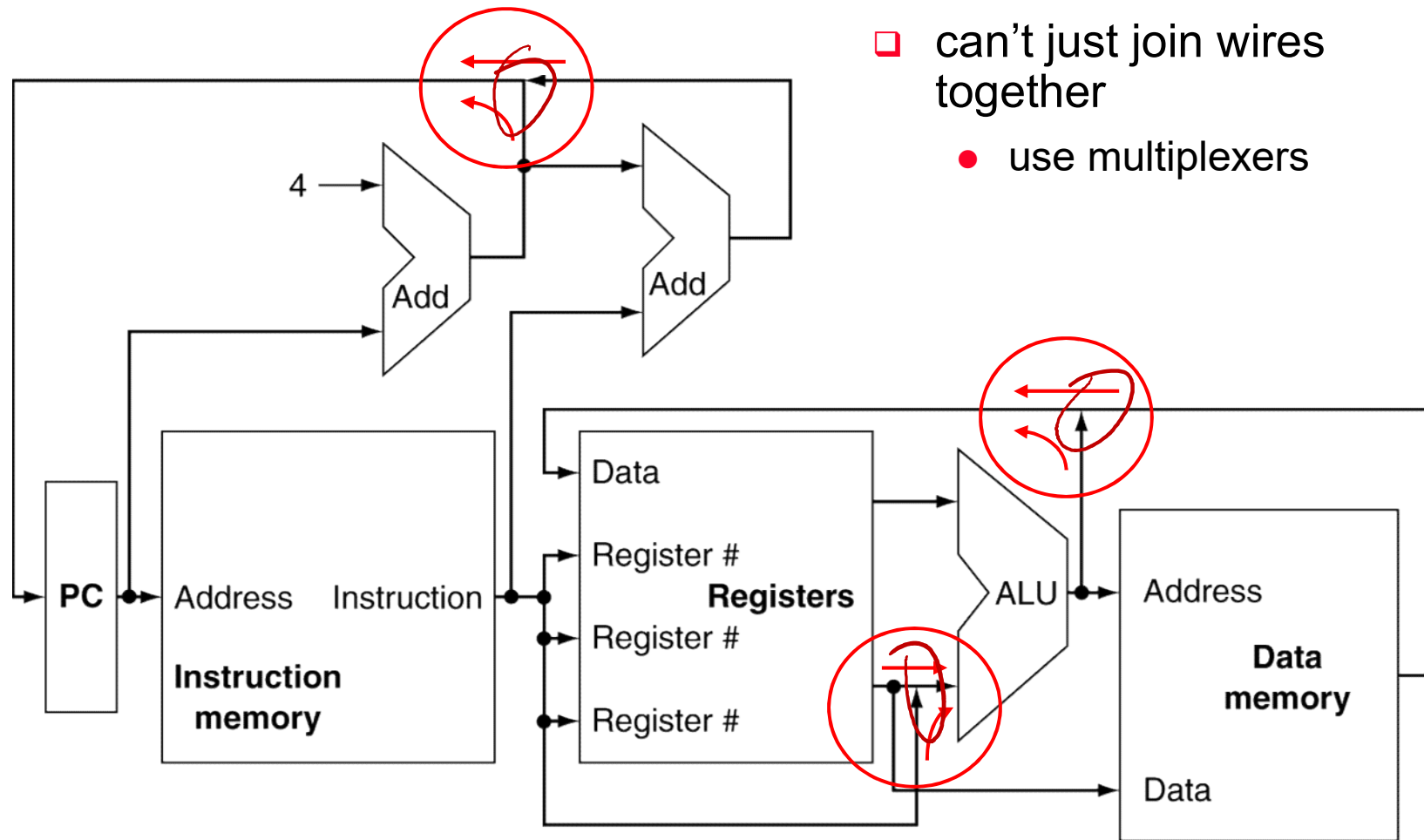

Building a Datapath

❑ datapath

- elements that process data and addresses in the CPU
 - registers, ALUs, mux's, memories, ...


❑ we will build a MIPS datapath incrementally

- refining the overview design

Fetching Instructions

□ fetching instructions involves

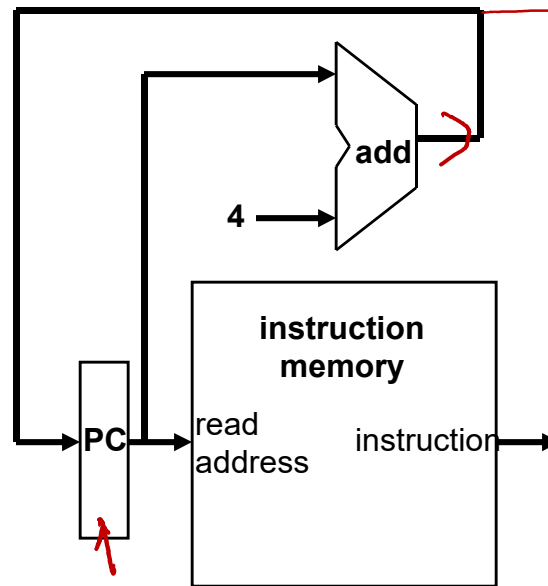- reading the instruction from instruction memory
- updating PC to hold the address of the next instruction




- PC is updated every cycle, so it does not need an explicit write control signal
- instruction memory is read every cycle, so it doesn't need an explicit read control signal

Decoding Instructions

❑ decoding instructions involves

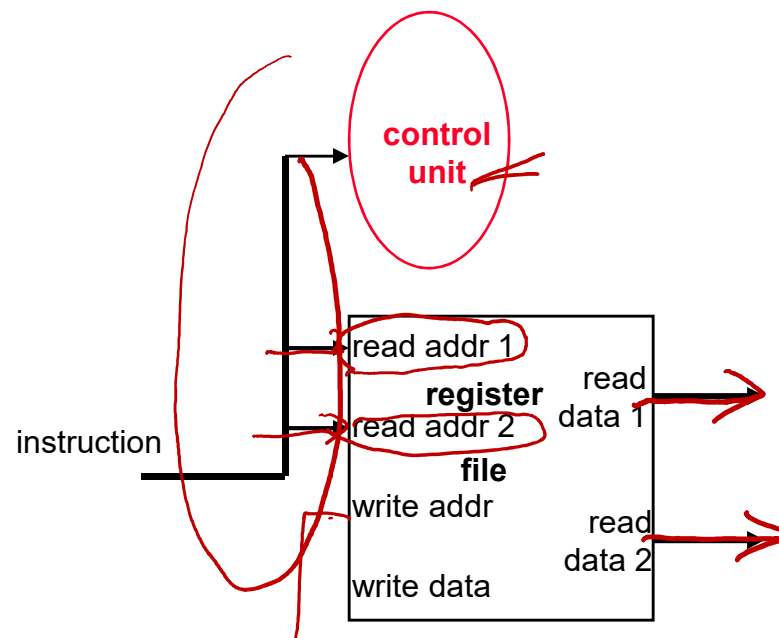
- sending the fetched instruction's opcode and function field bits to the control unit




- reading two values from register file
 - register file addresses are contained in the instruction

Executing R Format Operations

 - R format operations (**add, sub, slt, and, or**)



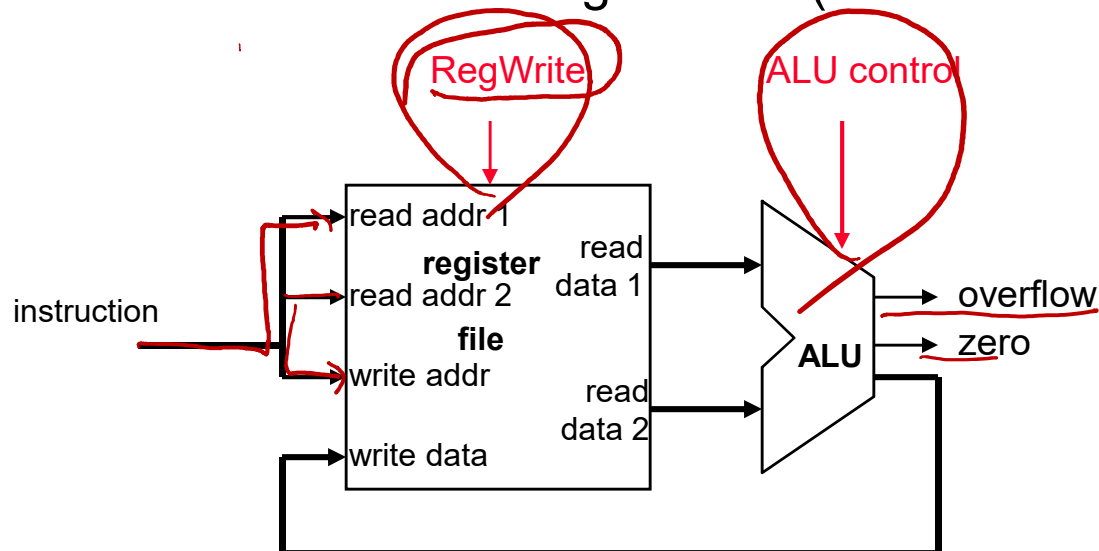- perform the (**op** and **funct**) operation on values in **rs** and **rt**
- store the result back into register file (into location **rd**)




- register file is not written every cycle (e.g. **sw**), so we need an explicit write control signal for register file

Executing Load and Store Operations

□ load and store operations involves

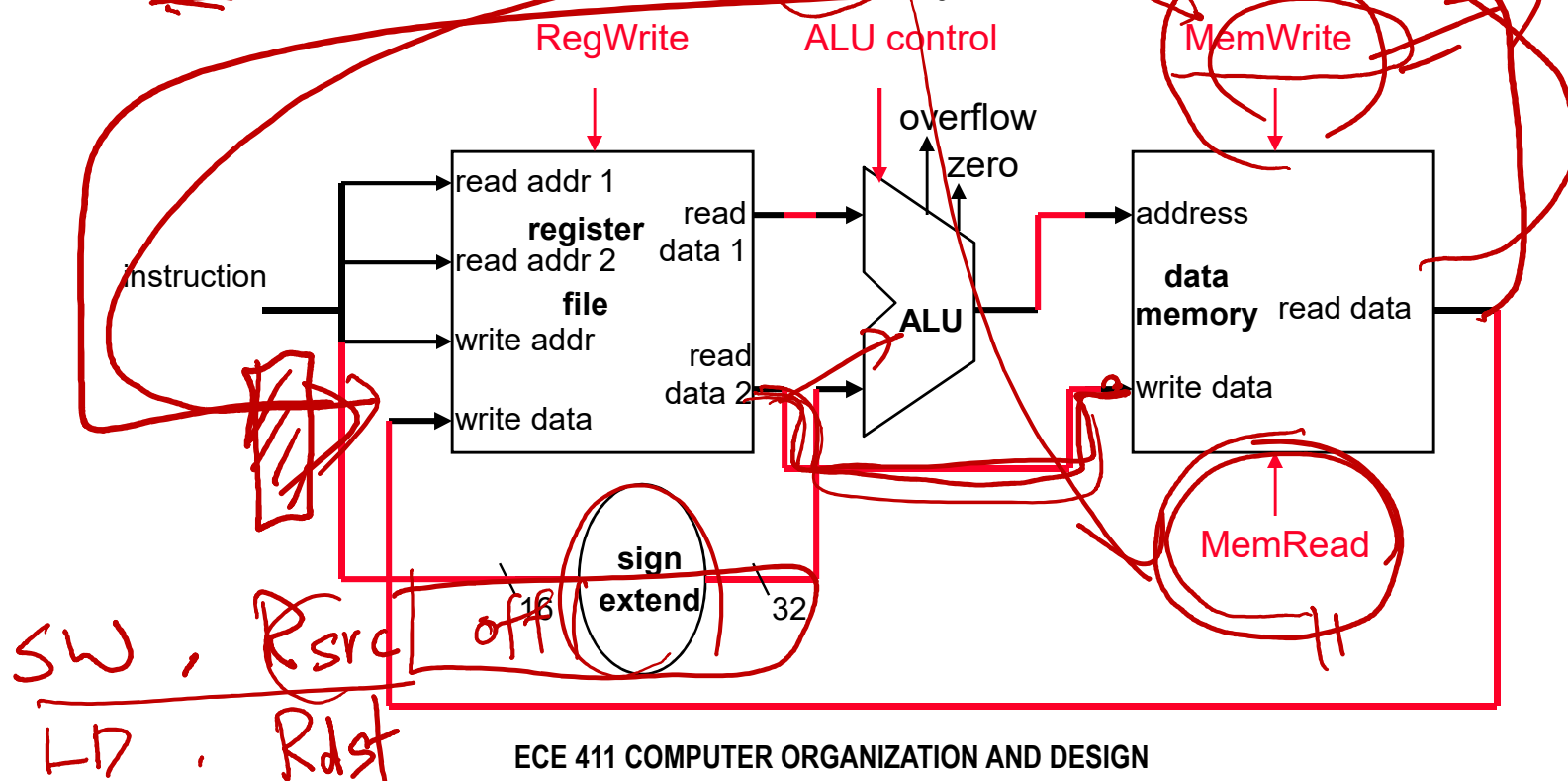
- compute memory address by adding the base register (read from register file during decode) to the 16-bit signed-extended offset field in the instruction
- **store** value (read from register file during decode) written to the data memory
- **load** value, read from data memory, written to register file



Executing Branch Operations

❑ branch operations involves

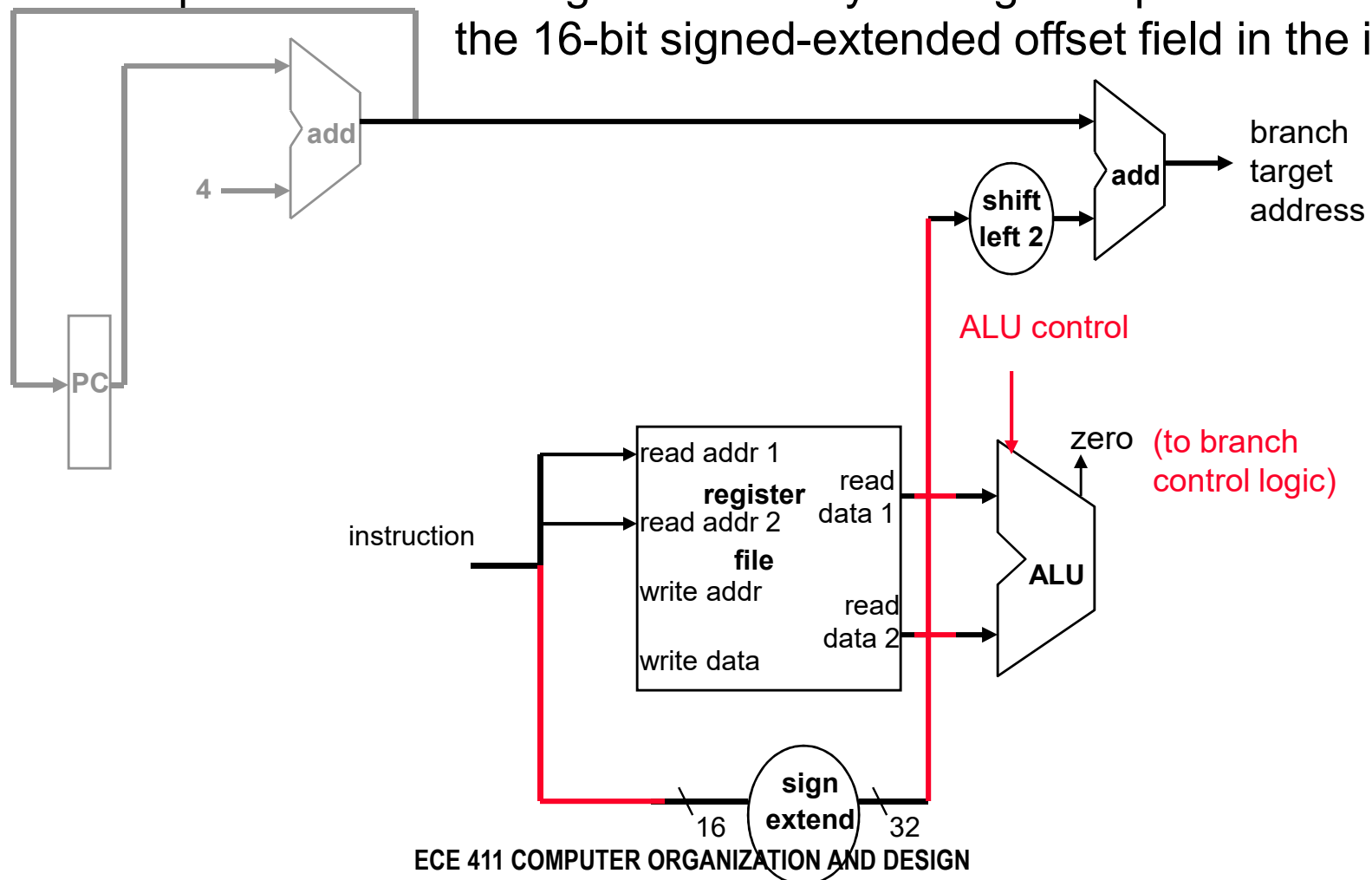
- compare the operands read from register file during decode for equality (**zero** ALU output)
- compute the branch target address by adding the updated PC to the 16-bit signed-extended offset field in the instr



Executing Jump Operations

❑ jump operation involves

 
- replace the lower 28 bits of the PC with the lower 26 bits of the fetched instruction shifted left by 2 bits



Creating a Single Datapath from the Parts

- ❑ assemble the datapath segments and add control lines and multiplexors as needed
- ❑ **single cycle** design – fetch, decode and execute each instructions in **one** clock cycle
 - no datapath resource can be used more than once per instruction, so some must be duplicated (e.g., separate instruction memory and data memory, several adders)
 - **multiplexors** needed at the input of shared elements with control lines to do the selection
 - write signals to control writing to the register file and data memory
- ❑ cycle time is determined by length of the longest path

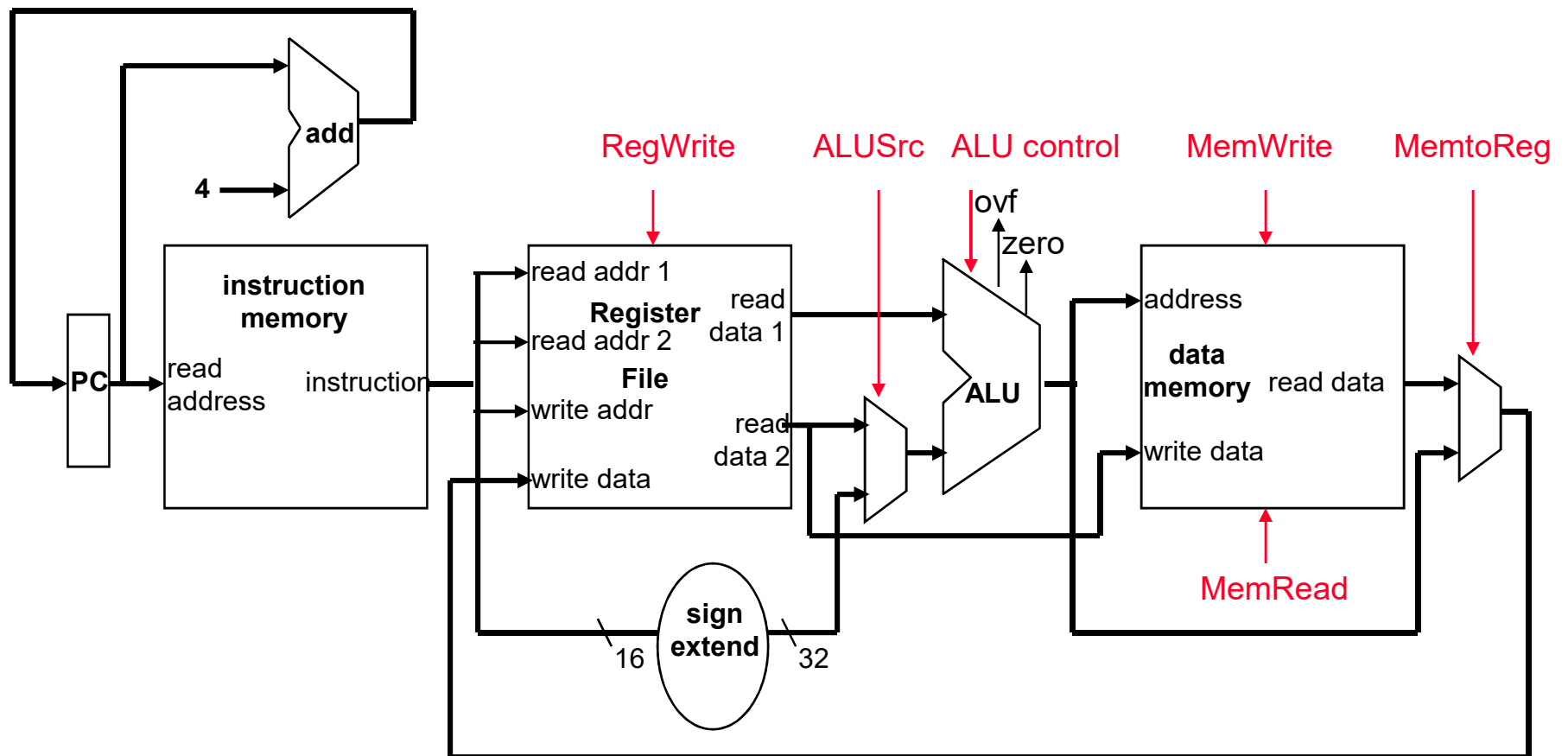Control signals for Fetch, Reg, and Memory




what determines the values needed on these control signals?

Adding the Control

*skip now
need to see*

 
- ❑ selecting the operations to perform (ALU, register file and memory read/write)
- ❑ controlling the flow of data (multiplexor inputs)



❑ observations


- op field **always** in bits 31-26
- addr of registers to be read are **always** specified by the rs field (bits 25-21) and rt field (bits 20-16); for lw and sw rs is the base register
- addr. of register to be written is in one of **two** places – in rt (bits 20-16) for lw; in rd (bits 15-11) for R-type instructions
- offset for beq, lw, and sw **always** in bits 15-0

Single Cycle Datapath w/ Control Unit

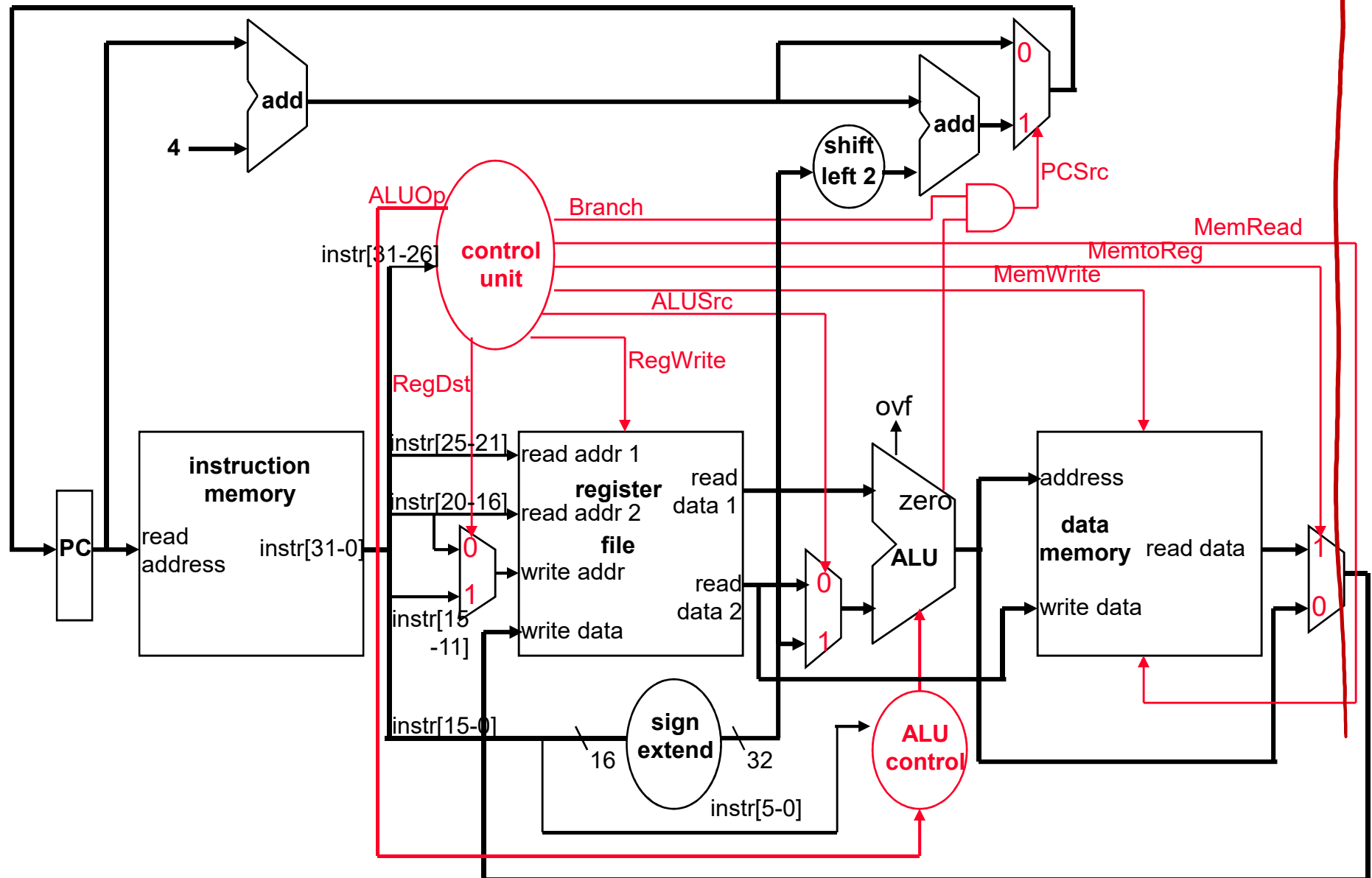


R-type Instruction Data/Control Flow


skip this now

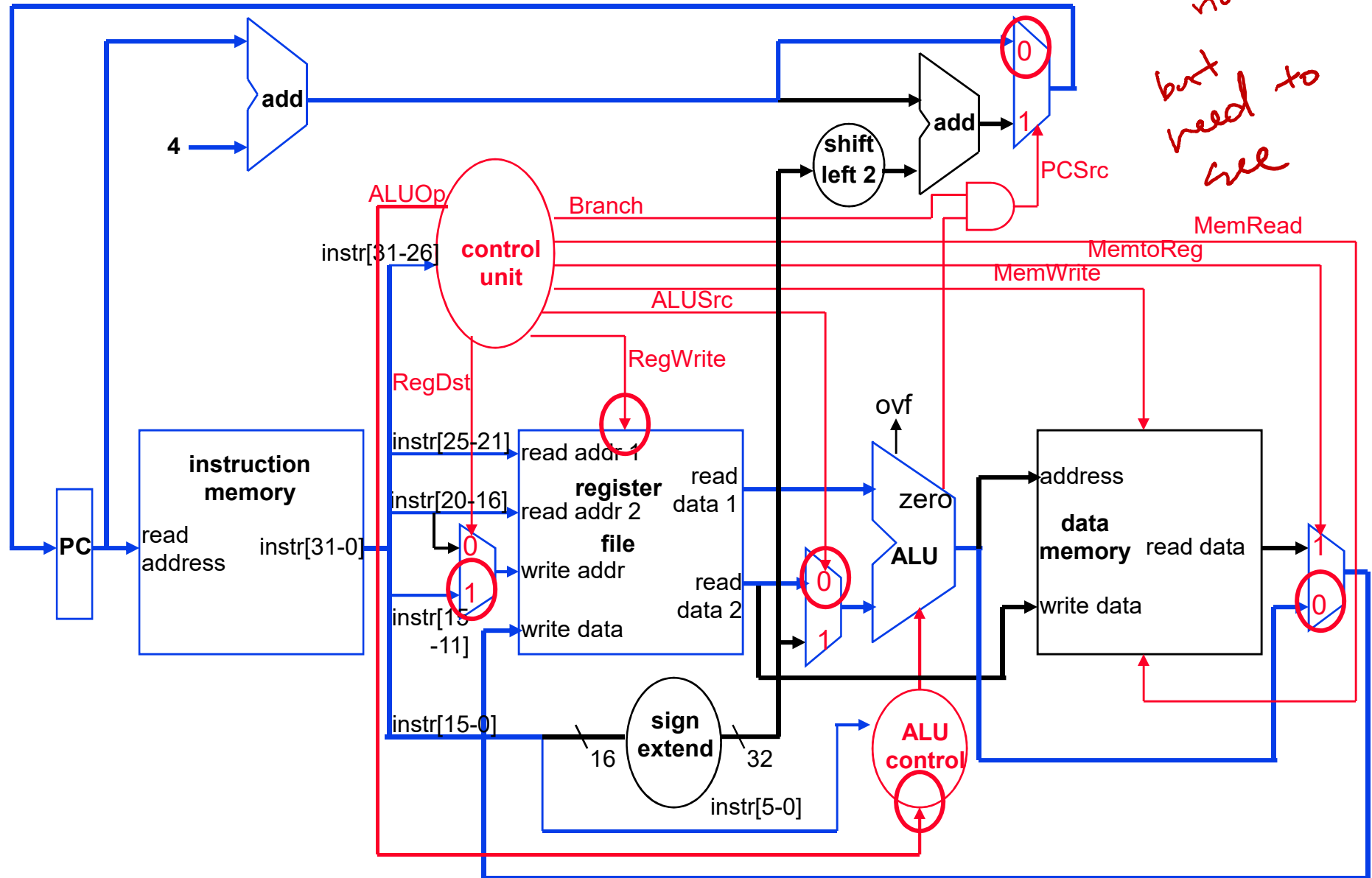


Load Word Instruction Data/Control Flow

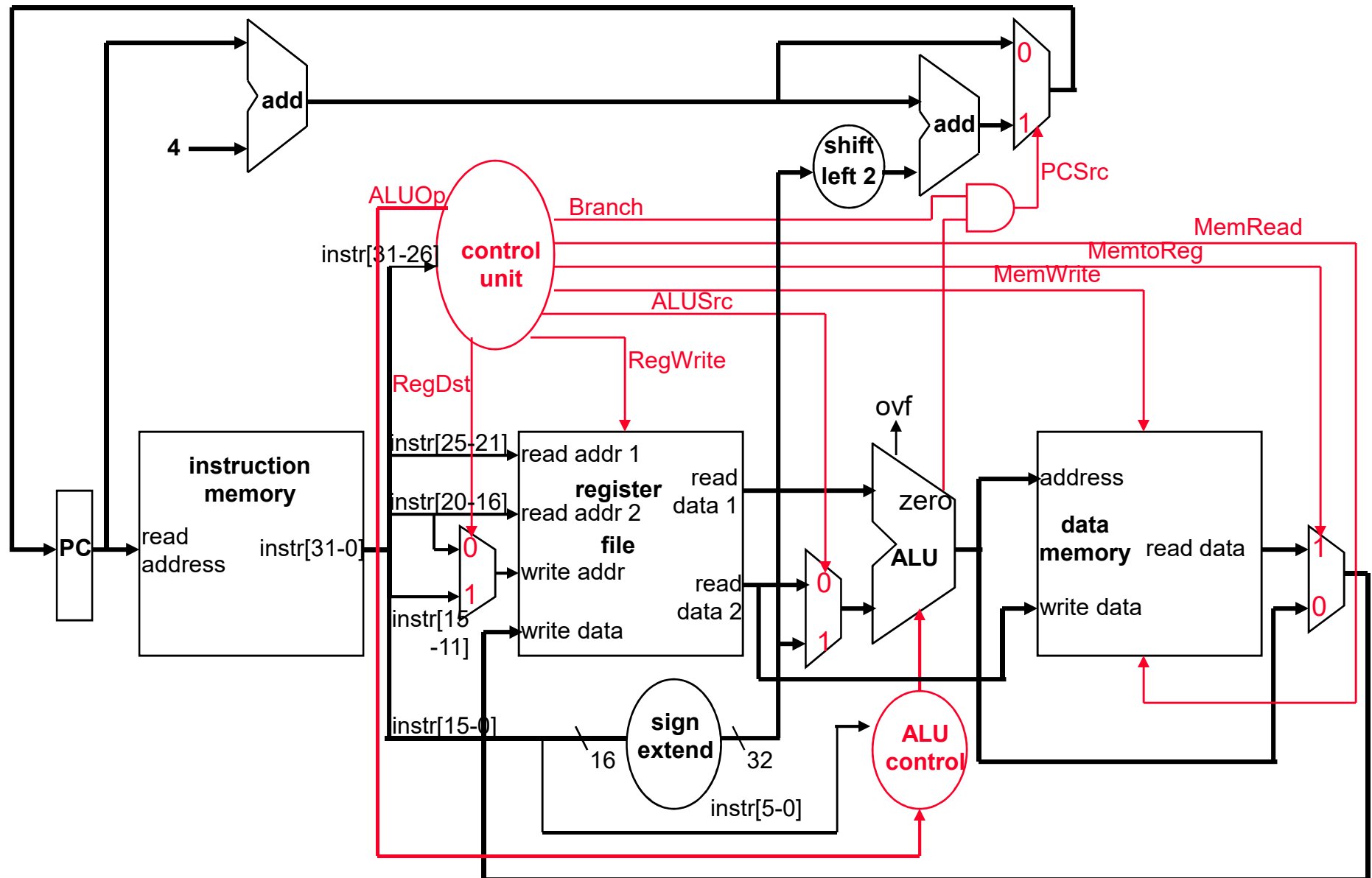


Load Word Instruction Data/Control Flow

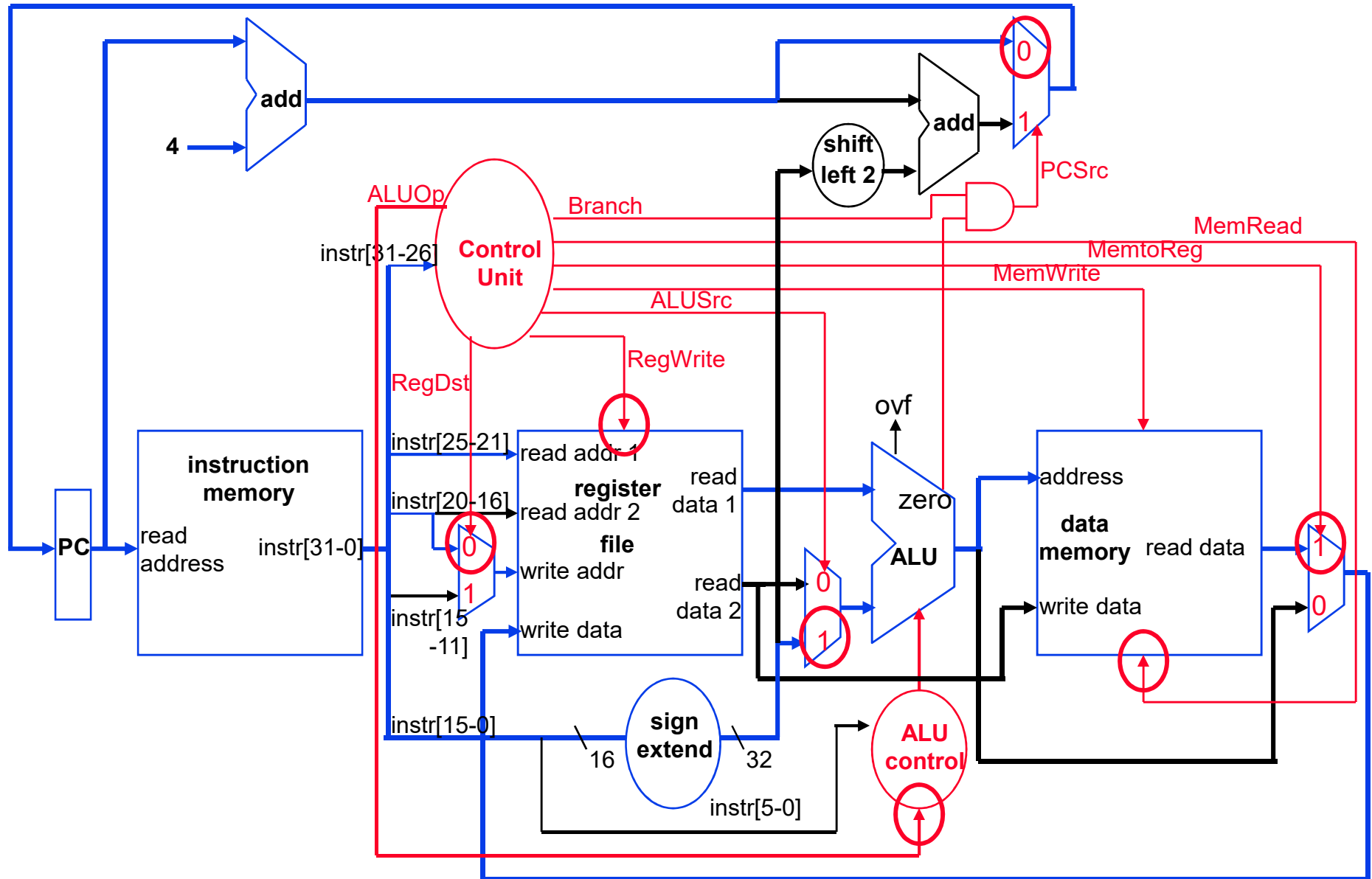


Branch Instruction Data/Control Flow

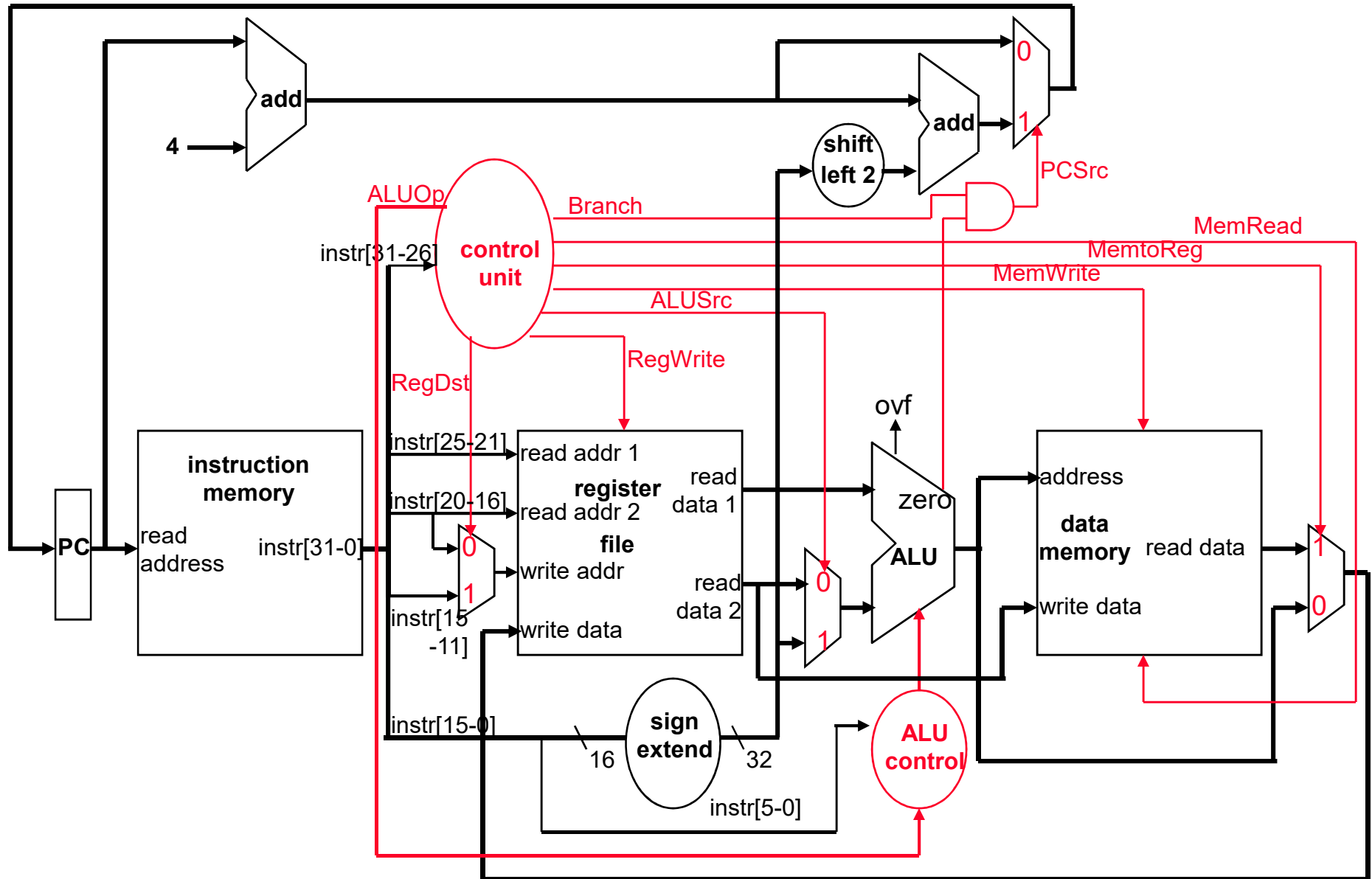


Branch Instruction Data/Control Flow

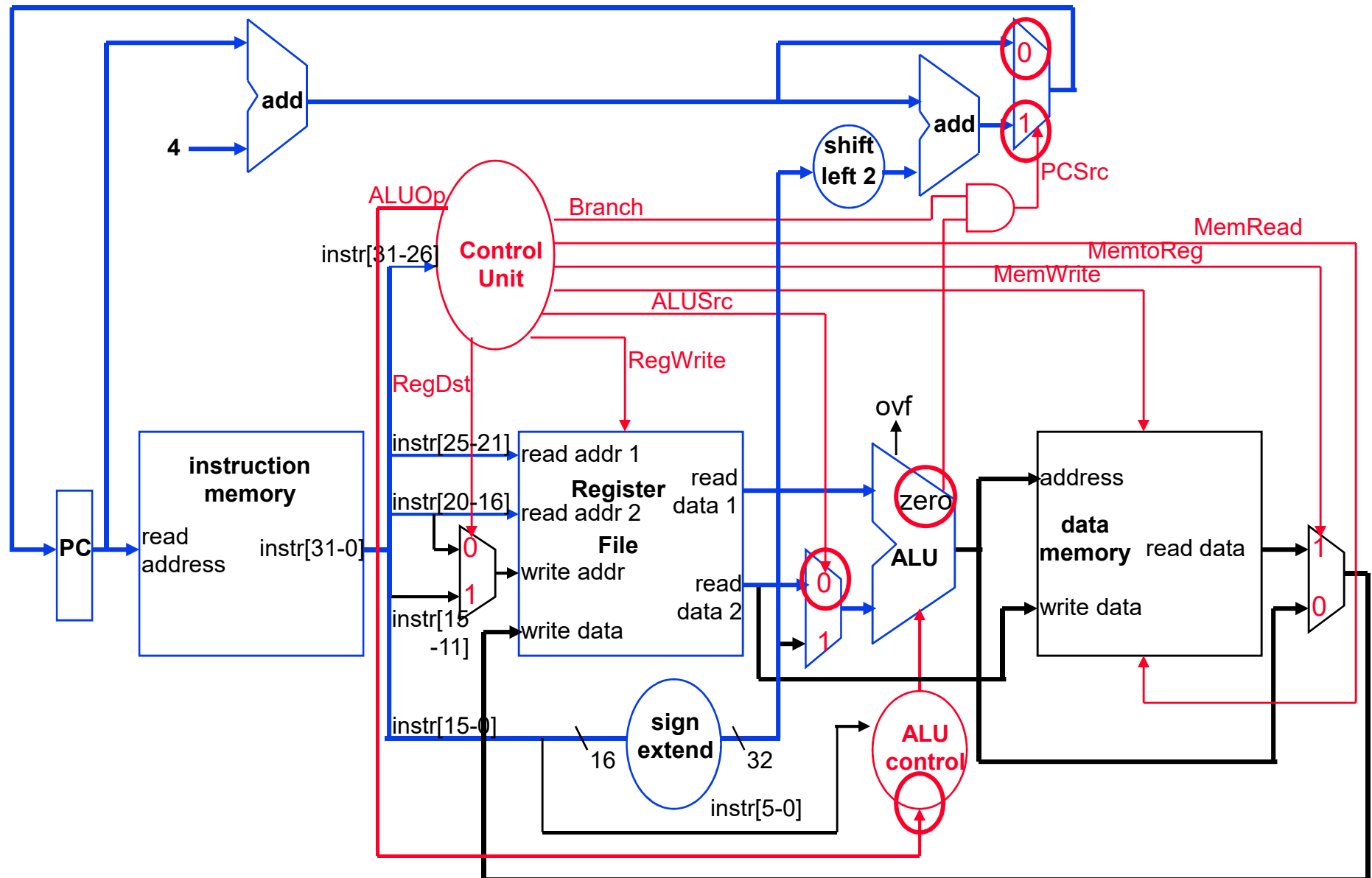

Adding the Jump Operation

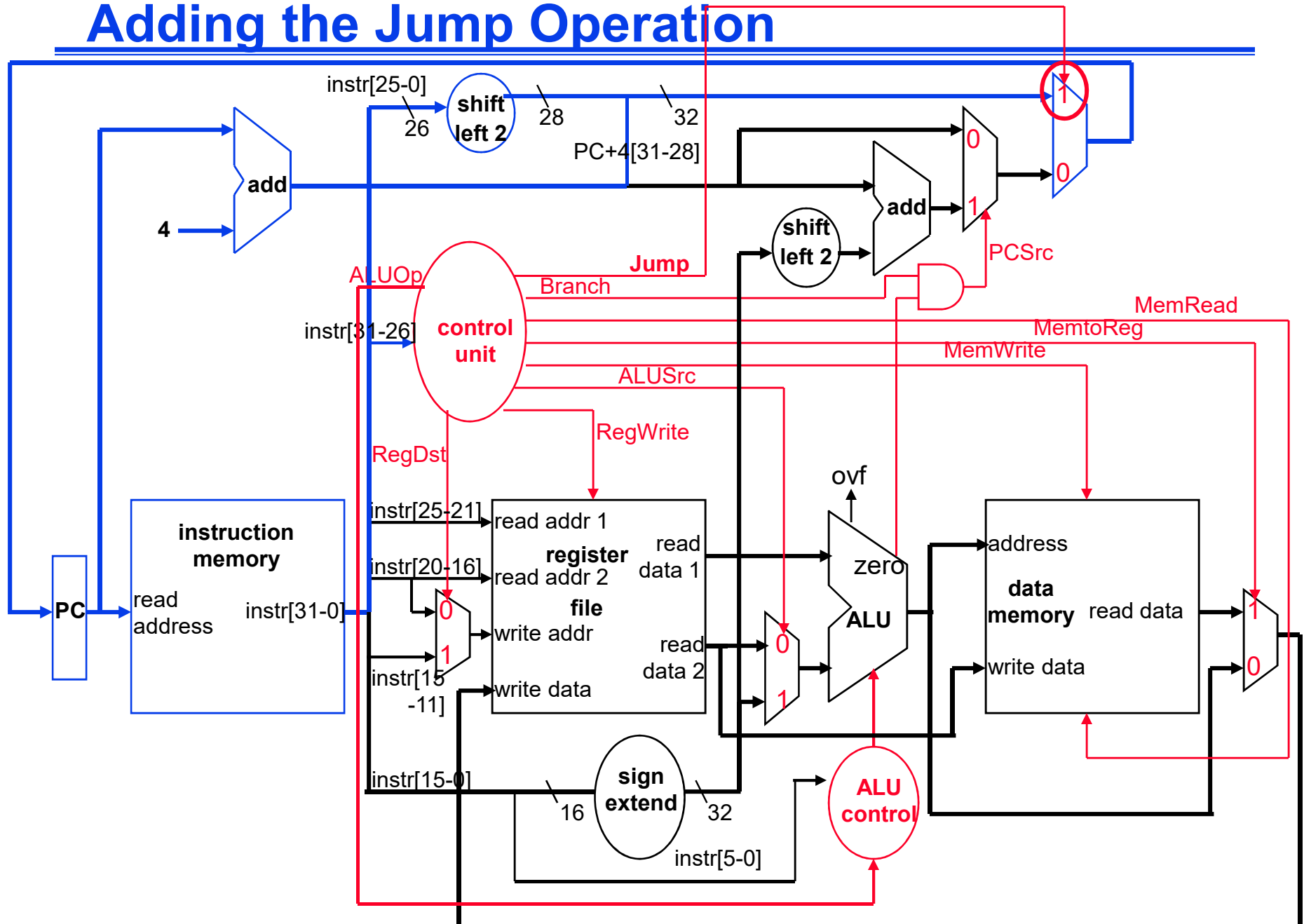

Instruction Type vs # of Required Cycles

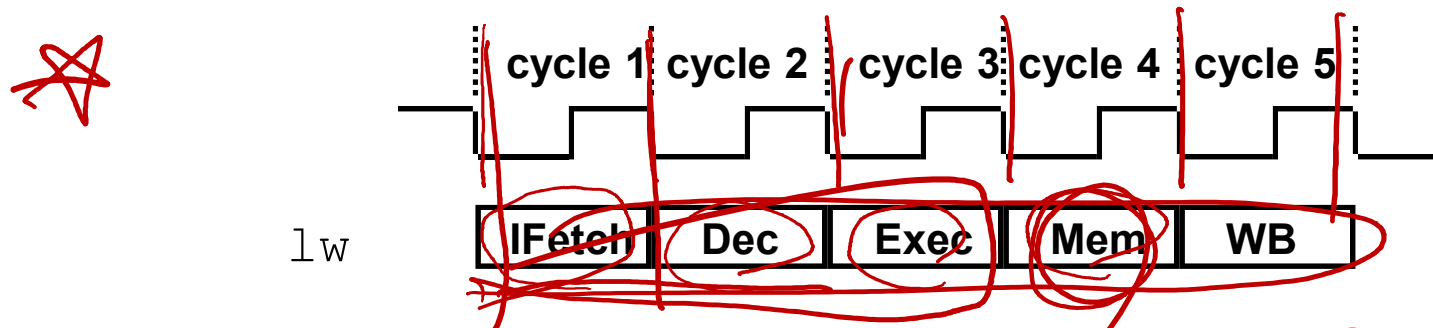


- ❑ IFetch: Instruction Fetch and Update PC
- ❑ Dec: Instruction Decode, Register Read, Sign Extend Offset
- ❑ Exec: Execute R-type; Calculate Memory Address; Branch Comparison; Branch and Jump Completion
- ❑ Mem: Memory Read; Memory Write Completion; R-type Completion (RegFile write)
- ❑ WB: Memory Read Completion (RegFile write)

→ INSTRUCTIONS TAKE FROM 3 - 5 CYCLES!

Single Cycle Disadvantages & Advantages

 - ❑ uses the clock cycle inefficiently – the clock cycle must be timed to accommodate the slowest instruction
 - especially problematic for more complex instructions like floating point multiply



- ❑ may be wasteful of area since some functional units (e.g., adders) must be duplicated since they can not be shared during a clock cycle

but

- ❑ is simple and easy to understand


Multicycle Datapath Approach

Look at the detail

- ❑ let an instruction take more than 1 clock cycle to complete
 - break up instructions into steps where each *step* takes a cycle while trying to
 - balance the amount of work to be done in each step
 - restrict each cycle to use only one major functional unit
 - not every instruction takes the *same* number of clock cycles
- ❑ in addition to *faster* clock rates, multicycle allows functional units that can be used more than once per instruction as long as they are used on *different* clock cycles, as a result
 - only need one memory – but only one memory access per cycle
 - need only one ALU/adder – but only one ALU operation per cycle

Multicycle Datapath Approach, con't

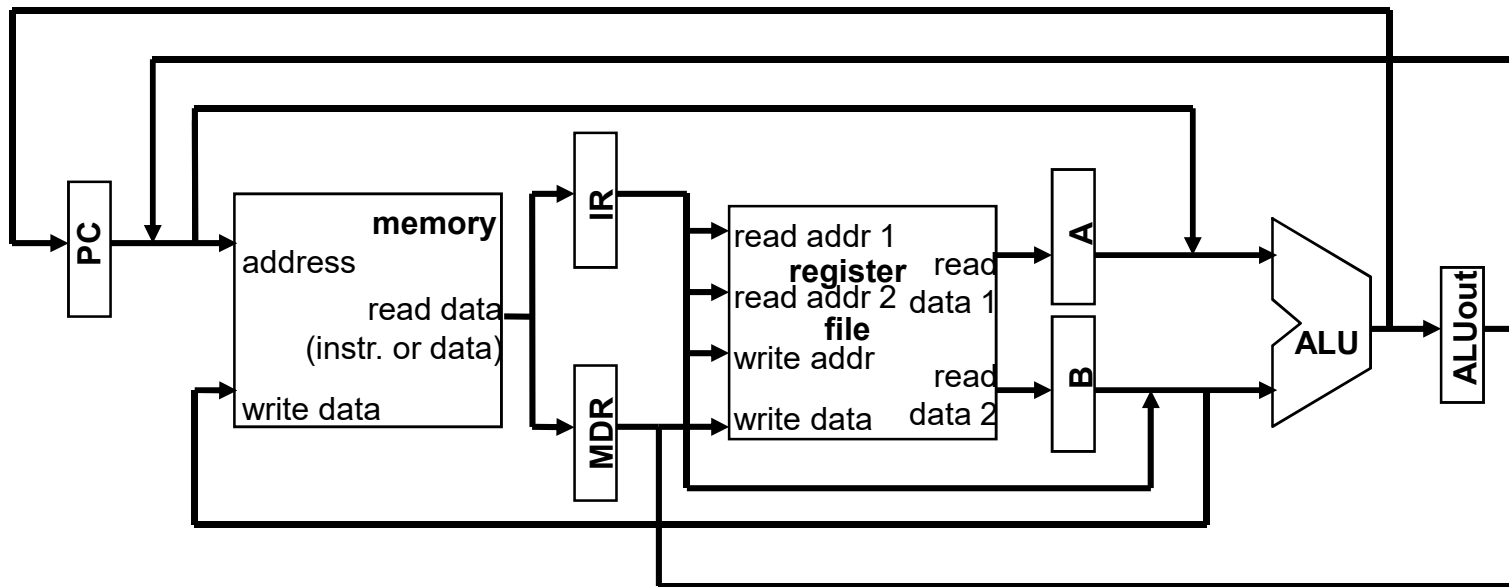- ❑ at the end of a cycle *you can have a look at this*
 - store values needed in a later cycle by the **current** instruction in an internal register (not visible to the programmer); all (except IR) hold data only b/w a pair of adjacent clock cycles (no write control signal needed)



IR – Instruction Register


MDR – Memory Data Register

A, B – regfile read data registers

ALUout – ALU output register


- data used by **subsequent** instructions are stored in programmer visible registers (i.e., register file, PC, or memory)

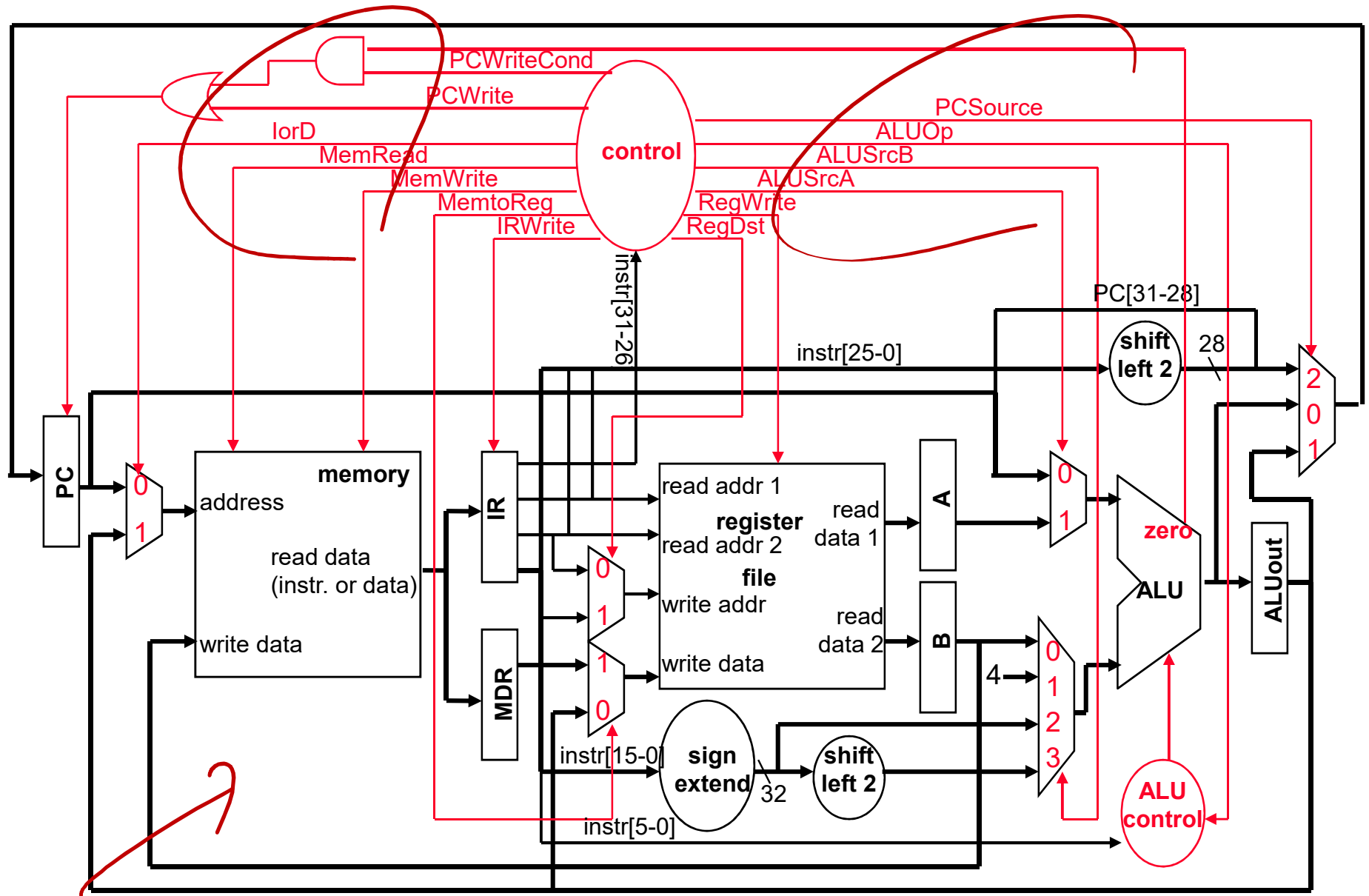The Multicycle Datapath w/ Control Signals




Multicycle Control Unit

- ❑ multicycle datapath control signals are not determined solely by the bits in the instruction
 - e.g., op code bits tell what operation the ALU should be doing, but *not* what instruction cycle is to be done next
- ❑ must use a finite state machine (FSM) for control
 - a set of states (current state stored in state register)
 - next state function (determined by current state and the input)
 - output function (determined by current state and the input)

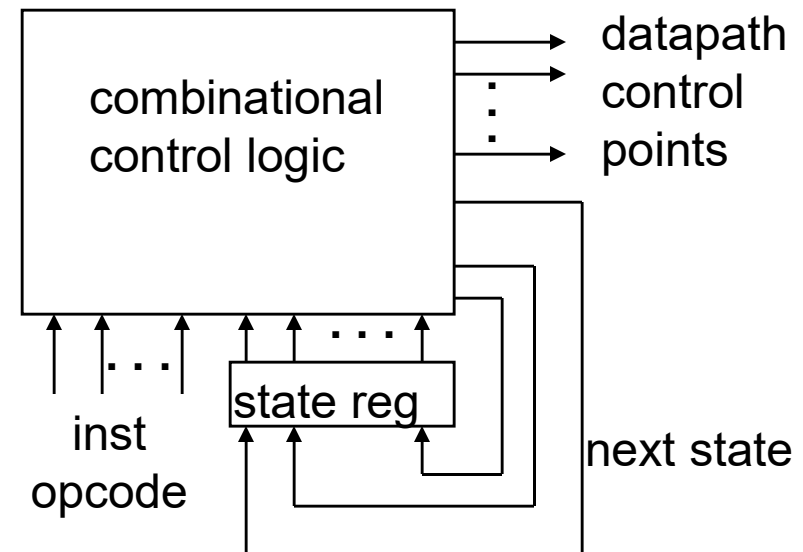

Multicycle Advantages & Disadvantages

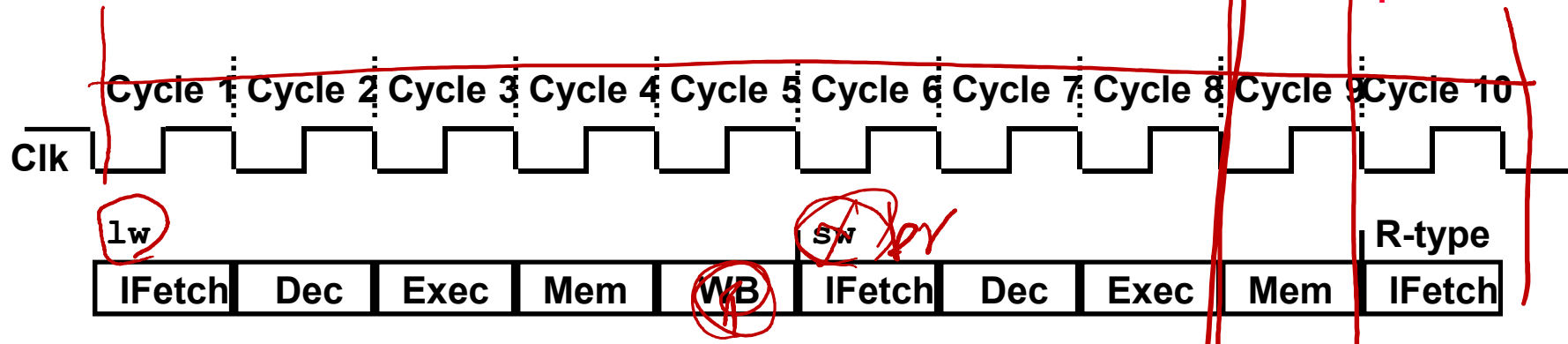- ❑ uses the clock cycle efficiently – the clock cycle is timed to accommodate the slowest instruction **step**




- ❑ multicycle implementations allow functional units to be used more than once per instruction as long as they are used on different clock cycles

but


- ❑ requires additional internal state registers, more muxes, and more complicated (FSM) control

Single Cycle vs. Multiple Cycle Timing

single cycle implementation:

 

multiple cycle implementation:

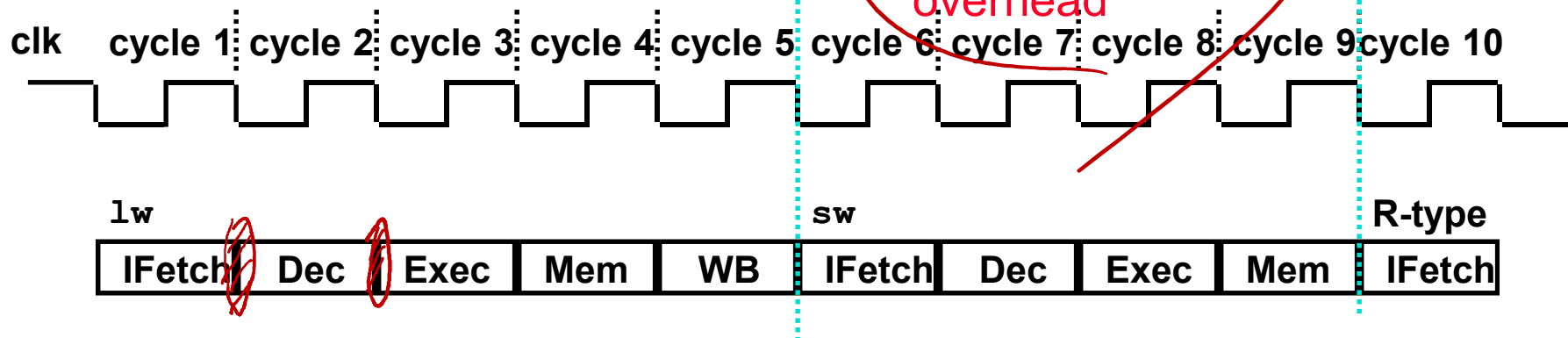

A Hypothetical Data Path Timing Analysis

- critical path: a path through combinational circuit that takes as long or longer than any other.

	I	Fetch	Decode R-Read	ALU	PC update	D Memory	R-Write	Total (ns)
Add		1	1	.9	-	-	.8	3.7
Load		1	1	.9	-	1	.8	4.7
Store		1	1	.9	-	1	-	3.9
beq		1	1	.9	.1	-	-	3.0

clock cycle time


$$= 4.7\text{ns} + t_{\text{setup}} + t_{\text{cq}}$$

T_{cycle}

A Hypothetical Data Path Timing Analysis

- critical path: a path through combinational circuit that takes as long or longer than any other

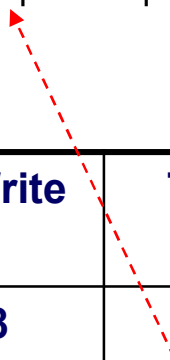clock cycle time
 $= 4.7\text{ns} + t_{\text{setup}} + t_{\text{cq}}$



	I	Fetch	Decode, R-Read	ALU	PC update	D Memory	R-Write	Total (ns)
Add		1	1	.9	-	-	.8	3.7
Load		1	1	.9	-	1	.8	4.7
Store		1	1	.9	-	1	-	3.9
beq		1	1	.9	.1	-	-	3.0

Cycle Time vs. CPI

- goal: balance amount of work done each cycle
 - ✓ load needs 5 cycles
 - ✓ add and store need 4
 - ✓ beq needs 3

single cycle
multi-cycles

	Fetch	Decode, R-Read	ALU	PC update	D Memory	R-Write	Total (ns)
Add	1	1	.9	-	-	.8	3.7
Load	1	1	.9	-	1	.8	4.7 <i>ns</i>
Store	1	1	.9	-	1	-	3.9
beq	1	1	.9	.1	-	-	3.0

Will multicycle design be faster?

- let's assume $t_{\text{setup}} + t_{\text{cq}}$ time for registers = 0.1 ns
 - ✓ single cycle design:
 - clock cycle time = $4.7 + 0.1 = 4.8$ ns
 - time/inst = 1 cycle/inst \times 4.8 ns/cycle = 4.8 ns/inst
 - ✓ multicycle design:
 - clock cycle time = $1.0 + 0.1 = 1.1$
 - time/inst = CPI \times 1.1 ns/cycle (depends on the types or mixture of instructions!)

	I	Fetch	Decode, R-Read	ALU	PC update	D Memory	R-Write	Total (ns)
Add		1	1	.9	-	-	.8	3.7
Load		1	1	.9	-	1	.8	4.7
Store		1	1	.9	-	1	-	3.9
beq		1	1	.9	.1	-	-	3.0

Will multicycle design be faster?

- let's assume $t_{\text{setup}} + t_{\text{cq}}$ time for the register = 0.1 ns

✓ single cycle design:

- clock cycle time = $4.7 + 0.1 = 4.8$ ns
- time/inst = $1 \text{ cycle/inst} \times 4.8 \text{ ns/cycle} = 4.8 \text{ ns/inst}$

✓ multicycle design:

- clock cycle time = $1.0 + 0.1 = 1.1$ ns
- time/inst = $\text{CPI} \times 1.1 \text{ ns/cycle}$

$$\Rightarrow \underline{4.1 \times 1.1}$$

	Cycles needed	Instruction frequency
Add	4	60%
Load	5	20%
Store	4	10%
beq	3	10%

$$\begin{aligned}
 & \text{CPI} = 4 \times 0.6 + 5 \times 0.2 + 4 \times 0.1 + 3 \times 0.1 \\
 & = 2.4 + 1.0 + 0.4 + 0.3 \\
 & = 4.1
 \end{aligned}$$

A More Extreme Example

*You can do this
on your own*

- calculation assumptions:
 - ✓ most instructions take 10 nanoseconds (ns)
 - ✓ but multiply instruction takes 40ns
 - ✓ multiplies are 10% of all instructions
- how much faster is a multi-cycle data path over a single-cycle data path?
 - ✓ for simplicity, assume $t_{\text{setup}} + t_{\text{cq}} = 0$
 - single-cycle time/inst = 40ns
 - multi-cycle with 10ns clock, time/inst = $(1 \times 0.9 + 4 \times 0.1) \times 10 = 13\text{ns}$

✓

Announcement

- next lecture: pipeline (overview)
 - ✓ Ch. 4.5 – 4.6 (HP1)
- MP assignment
 - ✓ MP1 checkpoint 1 due on 1/28 5pm